

### Exercise 30.4 - Enhanced - with Feedback

1 of 14

✓ Complete

Review | Constants

A solenoidal coil with 25 turns of wire is wound tightly around another coil with 350 turns. The inner solenoid is 21.0 cm long and has a diameter of 2.30 cm. At a certain time, the current in the inner solenoid is 0.150 A and is increasing at a rate of 1800 A/s.

#### Part A

For this time, calculate the average magnetic flux through each turn of the inner solenoid.

Express your answer in webers.

$$\Phi_B = 1.3 \times 10^{-7} \text{ Wb}$$

Submit

[Previous Answers](#)

✓ Correct

#### Part B

For this time, calculate the mutual inductance of the two solenoids.

Express your answer in henries.

$$M = 2.2 \times 10^{-5} \text{ H}$$

▼ **Part C**



For this time, calculate the emf induced in the outer solenoid by the changing current in the inner solenoid.

**Express your answer in volts.**

### Exercise 30.11 - Enhanced - with Solution

A metallic laboratory spring is typically 5.00 cm long and 0.150 cm in diameter and has 50 coils.

For related problemsolving tips and strategies, you may want to view a Video Tutor Solution of [Calculating self-induced emf](#).

#### Part A

If you connect such a spring in an electric circuit, how much self-inductance must you include for it if you model it as an ideal solenoid?

Express your answer with the appropriate units.



The input field consists of a text entry box labeled "Value" and a dropdown menu labeled "Units". Above the input field is a toolbar with various icons: a fraction icon, a Greek letter symbol, a left arrow, a right arrow, a refresh icon, a keyboard icon, and a question mark icon.

$L =$

**Exercise 30.19 - Enhanced - with Solution**

In a proton accelerator used in elementary particle physics experiments, the trajectories of protons are controlled by bending magnets that produce a magnetic field of 4.30 T.

For related problemsolving tips and strategies, you may want to view a Video Tutor Solution of [Storing energy in an inductor](#).

**▼ Part A**

What is the magnetic-field energy in a  $15.0 \text{ cm}^3$  volume of space where  $B = 4.30 \text{ T}$ ?

**Express your answer with the appropriate units.**

$$U = 110 \text{ J}$$

**Exercise 30.30 - Enhanced - with Feedback**

An inductor with an inductance of  $6.00 \text{ H}$  and a resistance of  $8.00 \Omega$  is connected to the terminals of a battery with an emf of  $5.00 \text{ V}$  and negligible internal resistance.

**Part A**

Just after the circuit is completed, at what rate is the battery supplying electrical energy to the circuit?

Express your answer with the appropriate units.

  
 $P =$   **Submit** [Request Answer](#)**Part B**

When the current has reached its final steady-state value, how much energy is stored in the inductor?

Express your answer with the appropriate units.

  
 $U_L =$

▼ **Part C**

What is the rate at which electrical energy is being dissipated in the resistance of the inductor?

**Express your answer with the appropriate units.**

Value Units

$P_R =$  Value Units

**Submit**

[Request Answer](#)

▼ **Part D**

What is the rate at which the battery is supplying electrical energy to the circuit?

**Express your answer with the appropriate units.**

Value Units

$P_e =$  Value Units

**Exercise 30.36 - Enhanced - with Feedback**

The minimum capacitance of a variable capacitor in a radio is 4.11 pF.

**Part A**

What is the inductance of a coil connected to this capacitor if the oscillation frequency of the  $L$ - $C$  circuit is 1.68 MHz, corresponding to one end of the AM radio broadcast band, when the capacitor is set to its minimum capacitance?

Express your answer in henries.

$L =$   H

**Submit**[Request Answer](#)**Part B**

The frequency at the other end of the broadcast band is 0.538 MHz. What is the maximum capacitance of the capacitor if the oscillation frequency is adjustable over the range of the broadcast band?

Express your answer in farads.

$C =$   F

**Exercise 30.40**

6 of 14

An  $L$ - $R$ - $C$  series circuit has  $L = 0.800 \text{ H}$ ,  $C = 3.00 \mu\text{F}$ , and  $R = 350.0 \Omega$ . At  $t = 0$  the current is zero and the initial charge on the capacitor is  $2.80 \times 10^{-4} \text{ C}$ .

**Review | Constants****Part A**

What is the value of the constant  $A$  in the following equation?

$$q = Ae^{-(R/2L)t} \cos \left( \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} t + \phi \right)$$

Express your answer with the appropriate units.

$A =$

**Submit**   [Previous Answers](#)   [Request Answer](#)

 **Incorrect; Try Again**

**Part B**

What is the value of the constant  $\phi$ ?

Express your answer in radians.

▼ Part C

How much time does it take for each complete current oscillation after the switch in this circuit is closed?

**Express your answer with the appropriate units.**

μA ↶ ↷ ⟳ ⌨ ?

$t =$  Value Units

**Submit**

[Request Answer](#)

▼ Part D

What is the charge on the capacitor after the first complete current oscillation?

**Express your answer with the appropriate units.**

μA ↶ ↷ ⟳ ⌨ ?

$q =$  Value Units

**Problem 30.45**

Magnetic fields within a sunspot can be as strong as 0.4 T. (By comparison, the earth's magnetic field is about 1/10,000 as strong.) Large sunspots can be as much as 25,000 km in radius. The material in a sunspot has a density of about  $3 \times 10^{-4} \text{ kg/m}^3$ .

**Part A**

If 100% of the magnetic field energy stored in a sunspot could be used to eject the sunspot's material away from the sun's surface, at what speed would that material be ejected? (Hint: Calculate the kinetic energy the magnetic field could supply to 1 m<sup>3</sup> of sunspot material.)

Express your answer in meters per second.

■  $\sqrt[3]{\square}$ AΣΦ↶↷⟳⌨?  
 $v =$   m/s

**Submit**[Request Answer](#)

**Problem 30.46**

◀ 8 of 14 ▶

A small solid conductor with radius  $a$  is supported by insulating, nonmagnetic disks on the axis of a thin-walled tube with inner radius  $b$ . The inner and outer conductors carry equal currents  $i$  in opposite directions.

**Review | Constants****Part A**

Use Ampere's law to find the magnetic field at any point at the distance  $r$  from the axis of the cable in the volume between the conductors.

Express your answer in terms of some or all of the variables  $a$ ,  $b$ ,  $i$ ,  $r$ , and constants  $\mu_0$ ,  $\pi$ .

$$B = \frac{\mu_0 i}{2\pi r}$$

**Submit**[Previous Answers](#)**Correct****Part B**

Write the expression for the flux  $d\Phi_B$  through a narrow strip of length  $l$  parallel to the axis, of width  $dr$ , at a distance  $r$  from the axis of the cable and lying in a plane containing the axis.

Express your answer in terms of some or all of the variables  $a$ ,  $b$ ,  $i$ ,  $l$ ,  $r$ ,  $dr$ , and constants  $\mu_0$ ,  $\pi$ .

$$d\Phi_B = \frac{\mu_0 i l dr}{2\pi r}$$

**Submit**[Previous Answers](#)

▼ Part C



Integrate your expression from part B over the volume between the two conductors to find the total flux produced by a current  $i$  in the central conductor.

Express your answer in terms of some or all of the variables  $a, b, i, l$ , and constants  $\mu_0, \pi$ .

$$\Phi_B = \frac{\mu_0 i l}{2\pi} \ln \left( \frac{b}{a} \right)$$

[Submit](#)

[Previous Answers](#)

**Correct**

▼ Part D

Find the inductance of a length  $l$  of the cable.

Express your answer in terms of some or all of the variables  $a, b, i, l$ , and constants  $\mu_0, \pi$ .



$L =$

[Submit](#)

[Request Answer](#)

▼ Part E

Use equation  $U = \frac{1}{2}LI^2$  to calculate the energy stored in the magnetic field for a length  $l$  of the cable.

Express your answer in terms of some or all of the variables  $a, b, i, l$ , and constants  $\mu_0, \pi$ .

■  $\sqrt[3]{\square}$  A $\Sigma\phi$  ↶ ↷ ⟳ ⌨️ ?

$U =$

[Submit](#)

[Request Answer](#)


**Problem 30.52**

◀ 9 of 14 ▶

An inductor with inductance  $L = 0.400 \text{ H}$  and negligible resistance is connected to a battery, a switch  $S$ , and two resistors,  $R_1 = 8.00 \Omega$  and  $R_2 = 5.00 \Omega$  (Figure 1). The battery has emf  $48.0 \text{ V}$  and negligible internal resistance.  $S$  is closed at  $t = 0$ .

**Review | Constants****Figure**

◀ 1 of 1 ▶

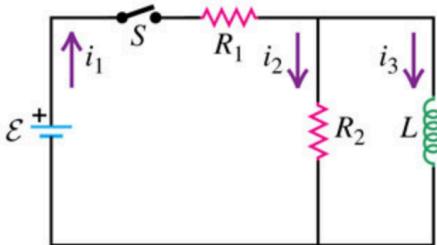**Part A**

What is the current  $i_1$  just after  $S$  is closed?

Express your answer with the appropriate units.

$\frac{\text{A}}{\text{V}}$	$\mu\text{A}$	↶	↷	⟳	⌨	?
-----------------------------	---------------	---	---	---	---	---

$i_1 =$

**Submit** [Request Answer](#)

**Part B**

What is the current  $i_2$  just after  $S$  is closed?

Express your answer with the appropriate units.

$\frac{\text{A}}{\text{V}}$	$\mu\text{A}$	↶	↷	⟳	⌨	?
-----------------------------	---------------	---	---	---	---	---

$i_2 =$

▼ Part C

What is the current  $i_3$  just after  $S$  is closed?

Express your answer with the appropriate units.

A calculator-style input field with a light gray background. At the top, there is a row of icons: a fraction button, a micro-angstrom button ( $\mu\text{\AA}$ ), a left arrow, a right arrow, a refresh/circular arrow, a keyboard icon, and a question mark. Below this is a text input area starting with "i<sub>3</sub> =". This area is divided into two boxes: the left box contains the placeholder "Value" and the right box contains the placeholder "Units".

**Submit**

[Request Answer](#)

▼ Part D

What is  $i_1$  after  $S$  has been closed a long time?

Express your answer with the appropriate units.

A calculator-style input field with a light gray background. At the top, there is a row of icons: a fraction button, a micro-angstrom button ( $\mu\text{\AA}$ ), a left arrow, a right arrow, a refresh/circular arrow, a keyboard icon, and a question mark. Below this is a text input area starting with "i<sub>1</sub> =". This area is divided into two boxes: the left box contains the placeholder "Value" and the right box contains the placeholder "Units".

**Submit**

[Request Answer](#)

▼ Part E

What is  $i_2$  after  $S$  has been closed a long time?

Express your answer with the appropriate units.

Value   Units

□□□ μA ↶ ↷ ⟳ ⌨️ ?

**Submit**

[Request Answer](#)

▼ Part F

What is  $i_3$  after  $S$  has been closed a long time?

Express your answer with the appropriate units.

Value   Units

□□□ μA ↶ ↷ ⟳ ⌨️ ?


**Submit**

[Request Answer](#)

**Part G**

Apply Kirchhoff's rules to the circuit and obtain a differential equation for  $i_3(t)$ . Integrate the equation to obtain an equation for  $i_3$  as a function of the time  $t$  that has elapsed since  $S$  was closed.

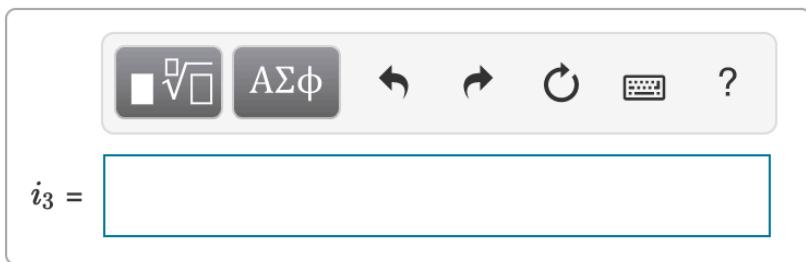**Express your answer in terms of the variables  $R_1$ ,  $R_2$ ,  $L$ ,  $\mathcal{E}$ , and  $t$ .**




A digital calculator interface with a light gray background. At the top, there is a row of buttons: a square root button ( $\sqrt{\square}$ ), a button labeled  $A\Sigma\phi$ , a left arrow, a right arrow, a circular refresh button, a keyboard icon, and a question mark icon. Below this row is a large input field containing the variable  $i_3 =$ . The entire interface is enclosed in a thin gray border.

**Submit**[Request Answer](#)**Part H**

Use the equation that you derived in part G to calculate the value of  $t$  for which  $i_3$  has half of the final value that you calculated in part F.

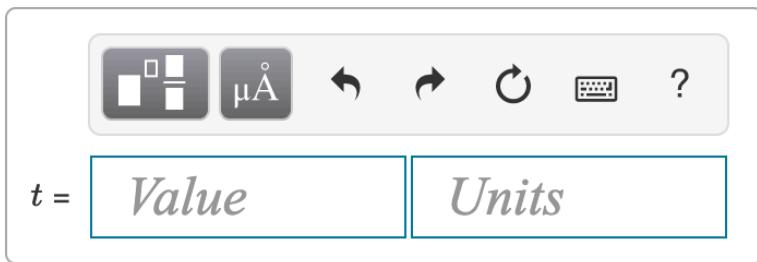**Express your answer with the appropriate units.**



A digital calculator interface with a light gray background. At the top, there is a row of buttons: a division button ( $\frac{\square}{\square}$ ), a button labeled  $\mu\text{A}$ , a left arrow, a right arrow, a circular refresh button, a keyboard icon, and a question mark icon. Below this row are two input fields: the first field contains the variable  $t =$  and the second field contains the word *Value*. The entire interface is enclosed in a thin gray border.

**Submit**[Request Answer](#)

▼ Part I

When  $i_3$  has half of its final value, what is  $i_2$ ?

Express your answer with the appropriate units.

Value Units

□□□ μΑ ↶ ↷ ⟳ ⌨️ ?

**Submit**

[Request Answer](#)

▼ Part J

When  $i_3$  has half of its final value, what is  $i_1$ ?

Express your answer with the appropriate units.

Value Units

□□□ μΑ ↶ ↷ ⟳ ⌨️ ?

**Submit**

[Request Answer](#)

**Problem 30.60 - Enhanced - with Feedback**

◀ 10 of 14 ▶

In the circuit shown in (Figure 1),  $S_1$  has been closed for a long enough time so that the current reads a steady  $3.50 \text{ A}$ . Suddenly,  $S_2$  is closed and  $S_1$  is opened at the same instant.

**Review | Constants****Part A**

What is the maximum charge that the capacitor will receive?

Express your answer in millicoulombs.


$$Q_{\max} = 0.350 \text{ mC}$$

**Submit**[Previous Answers](#)**Correct****Part B**

What is the current in the inductor at this time?

Express your answer in amperes.

□A $\Sigma\phi$ ↶↷⟳?i =A

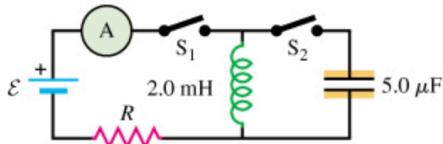**Submit**[Request Answer](#)


**Problem 30.61 - Enhanced - with Feedback**

◀ 11 of 14 ▶

In the circuit shown in (Figure 1),  $\mathcal{E} = 65.0 \text{ V}$ ,  $R_1 = 45.0 \Omega$ ,  $R_2 = 26.0 \Omega$ , and  $L = 0.291 \text{ H}$ . Switch  $S$  is closed at  $t = 0$ .

**Review | Constants****Figure**

◀ 1 of 1 ▶

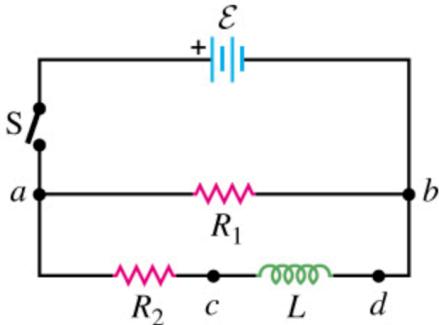**Part A**

Just after the switch is closed, what is the magnitude of the potential difference  $v_{ab}$  across the resistor  $R_1$ ?

Express your answer in volts.

$\sqrt[3]{\square}$ A $\Sigma\phi$ ↶↷⟳↹?  
 $v_{ab} =$   V

**Submit**[Request Answer](#)**Part B**

Which point,  $a$  or  $b$ , is at a higher potential?

- point  $a$   
 point  $b$

**Submit**[Request Answer](#)

▼ **Part C**

What is the magnitude of the potential difference  $v_{cd}$  across the inductor  $L$ ?

**Express your answer in volts.**

$$v_{cd} =$$

V

**Submit**

[Request Answer](#)

▼ **Part D**

Which point,  $c$  or  $d$ , is at a higher potential?

point  $c$

point  $d$

**Submit**

[Request Answer](#)

▼ **Part E**

The switch is left closed a long time and then opened. Just after the switch is opened, what is the magnitude of the potential difference  $v_{ab}$  across the resistor  $R_1$ ?

**Express your answer in volts.**

■  $\sqrt[3]{\square}$  AΣφ ↶ ↷ ⟳ ⌨ ?

$v_{ab} =$   V

**Submit**

[Request Answer](#)

▼ **Part F**

Which point,  $a$  or  $b$ , is at a higher potential?

point  $a$

point  $b$

**Submit**

[Request Answer](#)

▼ **Part G**

What is the magnitude of the potential difference  $v_{cd}$  across the inductor  $L$ ?

**Express your answer in volts.**

V AΣΦ ↶ ↷ ⟳ ⌨ ?

$v_{cd} =$   V

**Submit**

[Request Answer](#)

▼ **Part H**

Which point,  $c$  or  $d$ , is at a higher potential?

point  $c$

point  $d$


**Submit**

[Request Answer](#)

**Problem 30.63**

◀ 12 of 14 ▶

Consider the circuit shown in (Figure 1). Let  $\mathcal{E} = 36.0 \text{ V}$ ,  $R_0 = 50.0 \Omega$ ,  $R = 150 \Omega$ , and  $L = 4.00 \text{ H}$ .

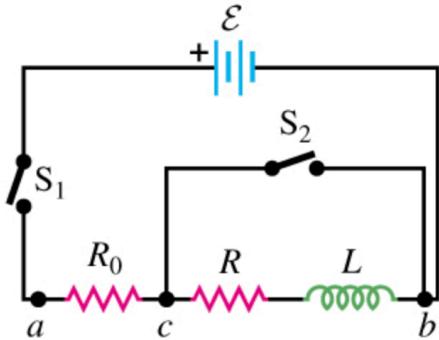**Review | Constants****Part A**

Switch  $S_1$  is closed and switch  $S_2$  is left open. Just after  $S_1$  is closed, what is the current  $i_0$  through  $R_0$ ?  
Express your answer in amperes.

$$i_0 = 0 \text{ A}$$

**Submit****Previous Answers****Correct****Part B**

Switch  $S_1$  is closed and switch  $S_2$  is left open. Just after  $S_1$  is closed, what is the potential difference  $V_{ac}$ ?  
Express your answer in volts.

$$V_{ac} = 0 \text{ V}$$

**Submit****Previous Answers****Correct**

▼ Part C

Switch  $S_1$  is closed and switch  $S_2$  is left open. Just after  $S_1$  is closed, what is the potential difference  $V_{cb}$ ?

Express your answer in volts.

■  $\sqrt{\square}$ AΣΦ↶↷⟳⌨?  
 $V_{cb} =$   V

**Submit**

[Request Answer](#)

▼ Part D

After  $S_1$  has been closed a long time ( $S_2$  is still open) so that the current has reached its final, steady value, what is  $i_0$ ?

Express your answer in amperes.

■  $\sqrt{\square}$ AΣΦ↶↷⟳⌨?  
 $i_0 =$   A

**Submit**

[Request Answer](#)

▼ Part E

After  $S_1$  has been closed a long time ( $S_2$  is still open) so that the current has reached its final, steady value, what is  $V_{ac}$ ?

Express your answer in volts.

■  $\sqrt{\square}$  A $\Sigma\phi$  ↶ ↷ ⟳ ⌨ ?

$V_{ac} =$   V

**Submit**

[Request Answer](#)

▼ Part F

After  $S_1$  has been closed a long time ( $S_2$  is still open) so that the current has reached its final, steady value, what is  $V_{cb}$ ?

Express your answer in volts.

■  $\sqrt{\square}$  A $\Sigma\phi$  ↶ ↷ ⟳ ⌨ ?

$V_{cb} =$   V

▼ **Part G**

Find the expression for  $i_0$  as functions of the time  $t$  since  $S_1$  was closed. Your results should agree with part A when  $t = 0$  and with part D when  $t \rightarrow \infty$ .

- $0.180 (1 - e^{-0.020t})$
- $0.180 (1 + e^{-t/0.010})$
- $0.180 (1 + e^{-t/0.020})$
- $0.180 (1 - e^{-t/0.020})$

**Submit**

[Request Answer](#)

▼ **Part H**

Find the expression for  $V_{ac}$  as functions of the time  $t$  since  $S_1$  was closed. Your results should agree with part B when  $t = 0$  and with part E when  $t \rightarrow \infty$ .

- $9.0 (1 - e^{-0.020t})$
- $9.0 (1 - e^{-t/0.020})$
- $9.0 (1 + e^{-t/0.010})$
- $9.0 (1 + e^{-t/0.020})$

▼ Part I



Find the expression for  $V_{cb}$  as functions of the time  $t$  since  $S_1$  was closed. Your results should agree with part C when  $t = 0$  and with part F when  $t \rightarrow \infty$ .

- $9.0 (3.00 - e^{-t/0.010})$
- $9.0 (3.00 - e^{-t/0.020})$
- $9.0 (3.00 + e^{-0.020t})$
- $9.0 (3.00 + e^{-t/0.020})$

[Submit](#)


[Previous Answers](#)

**Correct**

**Problem 30.66 - Enhanced - with Feedback**

◀ 13 of 14 ▶


In the circuit shown in (Figure 1), neither the battery nor the inductors have any appreciable resistance, the capacitors are initially uncharged, and the switch  $S$  has been in position 1 for a very long time.

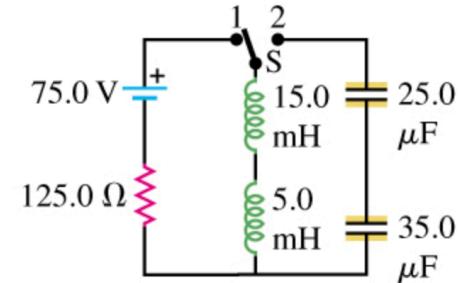**Figure****Review | Constants****Part A**

What is the current in the circuit?

Express your answer in amperes.

$$I = 0.600 \text{ A}$$

 **Submit**[Previous Answers](#)**Correct****Part B**

The switch is now suddenly flipped to position 2. Find the maximum charge that the  $25.0 \mu\text{F}$  capacitor will receive.  
Express your answer in coulombs.

$$q =$$

$$\text{C}$$

▼ Part C

The switch is now suddenly flipped to position 2. Find the maximum charge that the  $35.0 \mu\text{F}$  capacitor will receive.

**Express your answer in coulombs.**

◻  $\sqrt{\square}$  AΣφ ↶ ↷ ⟳ ⌨️ ?

$q =$    C

**Submit**

[Request Answer](#)

▼ Part D

How much time after the switch is flipped will it take the capacitors to acquire this charge?

**Express your answer in seconds.**

◻  $\sqrt{\square}$  AΣφ ↶ ↷ ⟳ ⌨️ ?


$t =$    s

**Submit**

[Request Answer](#)

**Review | Constants****Challenge Problem 30.71**

Consider the circuit shown in (Figure 1). Switch S is closed at time  $t = 0$ , causing a current  $i_1$  through the inductive branch and a current  $i_2$  through the capacitive branch. The initial charge on the capacitor is zero, and the charge at time  $t$  is  $q_2$ .

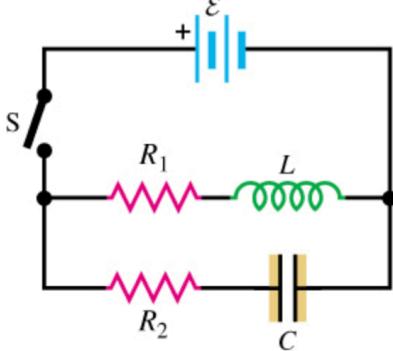**Figure****Part A**Derive expression for  $i_1$  as function of time.Express your answer in terms of some or all of the variables  $\mathcal{E}$ ,  $L$ ,  $C$ ,  $R_1$ ,  $R_2$ , and  $t$ .

$$\boxed{\sqrt{\frac{1}{L}} \text{ A} \Sigma \phi}$$

$$i_1 =$$

**Submit****Request Answer****Part B**Derive expression for  $i_2$  as function of time.Express your answer in terms of some or all of the variables  $\mathcal{E}$ ,  $L$ ,  $C$ ,  $R_1$ ,  $R_2$ , and  $t$ .

$$\boxed{\sqrt{\frac{1}{C}} \text{ A} \Sigma \phi}$$

$$i_2 =$$

▼ Part C

Derive expression for  $q_2$  as function of time.

**Express your answer in terms of some or all of the variables  $\mathcal{E}$ ,  $L$ ,  $C$ ,  $R_1$ ,  $R_2$ , and  $t$ .**

■  $\sqrt{\square}$ A $\Sigma\phi$ ↶↷⟳⌨?

**Submit**

[Request Answer](#)

▼ Part D

For the remainder of the problem let the circuit elements have the following values:  $\mathcal{E} = 43 \text{ V}$ ,  $L = 7.5 \text{ H}$ ,  $C = 27 \mu\text{F}$ ,  $R_1 = 29 \Omega$ , and  $R_2 = 4600 \Omega$ . What is the initial current through the inductive branch?

**Express your answer in amperes.**

■  $\sqrt{\square}$ A $\Sigma\phi$ ↶↷⟳⌨?  
 $i_L(0) =$   A

▼ Part E

What is the initial current through the capacitive branch?

**Express your answer in amperes.**

■  $\sqrt{\square}$  A $\Sigma\phi$  ↶ ↷ ⟳ ⌨️ ?

 $i_C(0) = \text{_____} \text{ A}$

**Submit**

[Request Answer](#)

▼ Part F

What is the current through the inductive branch a long time after the switch has been closed?

**Express your answer in amperes.**

■  $\sqrt{\square}$  A $\Sigma\phi$  ↶ ↷ ⟳ ⌨️ ?

 $i_L(\infty) = \text{_____} \text{ A}$

▼ **Part G**

What is the current through capacitive branch a long time after the switch has been closed?

**Express your answer in amperes.**

■  $\sqrt[3]{\square}$  AΣφ ↶ ↷ ⟳ ⌨ ?

 $i_C(\infty) =$   A

**Submit**

[Request Answer](#)

▼ **Part H**

At what time  $t_1$  (accurate to two significant figures) will the currents  $i_1$  and  $i_2$  be equal? (*Hint:* You might consider using series expansions for the exponentials.)

**Express your answer in seconds.**

■  $\sqrt[3]{\square}$  AΣφ ↶ ↷ ⟳ ⌨ ?

 $t_1 =$   s

## ▼ Part I

For the conditions given in part I, determine  $i_1$ .

**Express your answer in amperes.**

◻  $\sqrt{\square}$  A $\Sigma\phi$  ↶ ↽ ⟳ ⌨️ ?

$i_1 =$   A

**Submit**

[Request Answer](#)

## ▼ Part J

The total current through the battery is  $i = i_1 + i_2$ . At what time  $t_2$  (accurate to two significant figures) will  $i$  equal one-half of its final value? (*Hint:* The numerical work is greatly simplified if one makes suitable approximations. A sketch of  $i_1$  and  $i_2$  versus  $t$  may help you decide what approximations are valid.)

**Express your answer in seconds.**

◻  $\sqrt{\square}$  A $\Sigma\phi$  ↶ ↽ ⟳ ⌨️ ?

$t_2 =$   s