


Exercise 26.6 - Enhanced - with Feedback

1 of 10

For the circuit shown in (Figure 1) both meters are idealized, the battery has no appreciable internal resistance, and the ammeter reads 1.65 A.

Figure

1 of 1

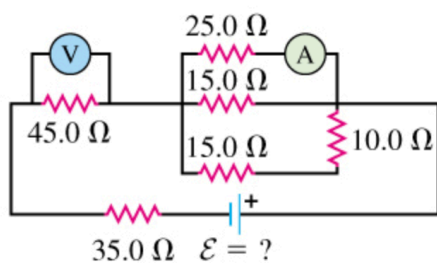

Review I Constants

Part A

What does the voltmeter read?

Express your answer in volts.

$\sqrt{\square}$ $\Delta \Sigma \Phi$ \leftarrow \rightarrow $\text{\textcircled{R}}$ $\text{\textcircled{K}}$ $?$

$V =$ V

Submit

[Request Answer](#)

Part B

What is the emf \mathcal{E} of the battery?

Express your answer in volts.


$\sqrt{\square}$ $\Delta \Sigma \Phi$ \leftarrow \rightarrow $\text{\textcircled{R}}$ $\text{\textcircled{K}}$ $?$

$\mathcal{E} =$ V

◀ 2 of 10 ▶

Review | Constants

1 of 1

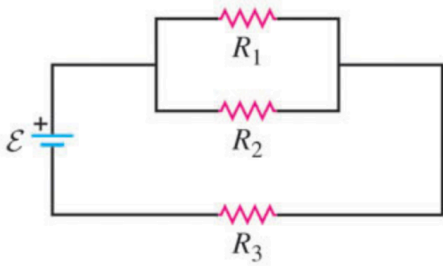

Express your answer with the appropriate units.

Previous Answers

Correct answer is shown. Your answer 13.33 A was either rounded differently or used a different number of significant figures than required for this part.

Express your answer with the appropriate units.

$$I_3 =$$



Value






Units

▼ **Part C**

What is the emf of the battery?

Express your answer with the appropriate units.





$\mathcal{E} =$

Submit

[Request Answer](#)


Exercise 26.18 - Enhanced - with Feedback

< 3 of 10 >

In the circuit shown in (Figure 1), $\mathcal{E} = 71.0 \text{ V}$, $R_1 = 4.00 \Omega$, $R_2 = 6.00 \Omega$, and $R_3 = 3.00 \Omega$.

Figure

< 1 of 1 >

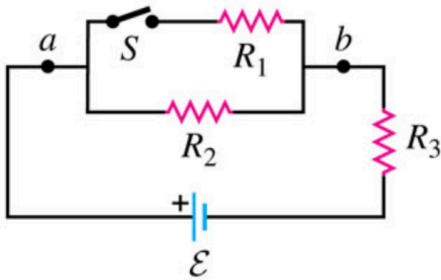

Review | Constants

▼ Part A

What is the potential difference V_{ab} between points a and b when the switch S is open?

Express your answer with the appropriate units.

$V_{ab} =$

Submit

[Request Answer](#)

▼ Part B

What is the potential difference V_{ab} between points a and b when the switch S is closed?



Express your answer with the appropriate units.






$V_{ab} =$

▼ **Part C**

For the $4.00\ \Omega$ resistor, calculate the current through the resistor with S open.

Express your answer with the appropriate units.





$I =$

Value

Units



Submit





[Request Answer](#)

▼ **Part D**

For the $4.00\ \Omega$ resistor, calculate the current through the resistor with S closed.

Express your answer with the appropriate units.





$I =$

Value

Units



Submit






[Request Answer](#)

▼ **Part E**

For the $6.00\ \Omega$ resistor, calculate the current through the resistor with S open.

Express your answer with the appropriate units.





$I =$



Submit






[Request Answer](#)

▼ **Part F**

For the $6.00\ \Omega$ resistor, calculate the current through the resistor with S closed.

Express your answer with the appropriate units.





$I =$



Submit






[Request Answer](#)

▼ Part G

For the $3.00\ \Omega$ resistor, calculate the current through the resistor with S open.

Express your answer with the appropriate units.





$I =$

Value

Units



Submit






[Request Answer](#)

▼ Part H

For the $3.00\ \Omega$ resistor, calculate the current through the resistor with S closed.

Express your answer with the appropriate units.





$I =$

Value

Units

Submit

[Request Answer](#)

▼ Part I

For each resistor, does the current increase or decrease when S is closed?

Drag the appropriate items to their respective bins.

Reset

Help

R_1

R_2

R_3

increases

decreases

Submit

[Request Answer](#)



Express your answer in amperes.

Submit [Request Answer](#)

▼ **Part B**








Express your answer in amperes.

$I =$ A

▼ **Part C**

Find the magnitude of current in the lower branch.

Express your answer in amperes.

$I =$

A








Submit

[Request Answer](#)

▼ **Part D**

What is the potential difference V_{ab} of point a relative to point b ?

Express your answer in volts.

$V_{ab} =$


V

Exercise 26.29 - Enhanced - with Solution

In the circuit shown in (Figure 1) the batteries have negligible internal resistance and the meters are both idealized. With the switch S open, the voltmeter reads 20.0 V.

For related problemsolving tips and strategies, you may want to view a Video Tutor Solution of [A complex network](#).

Figure 1 of 1

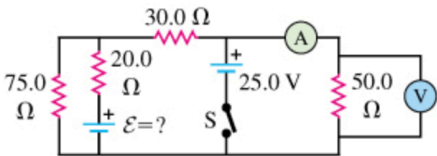

Review | Constants

Part A

Find the emf \mathcal{E} of the battery.
Express your answer in volts.

$\mathcal{E} =$ V

Submit Request Answer

Part B

What will the ammeter read when the switch is closed?
Express your answer in amperes.

$I =$ A

6 of 10

Review | Constants

1 of 1



$I =$	<i>Value</i>	<i>Units</i>
-------	--------------	--------------

Submit Request Answer

▼ **Part B**



$\varepsilon =$	<i>Value</i>	<i>Units</i>
-----------------	--------------	--------------

Exercise 26.41 - Enhanced - with Solution


7 of 10

In the circuit shown in (Figure 1) both capacitors are initially charged to 50.0 V.

For related problem-solving tips and strategies, you may want to view a Video Tutor Solution of [Discharging a capacitor](#).

Figure

1 of 1

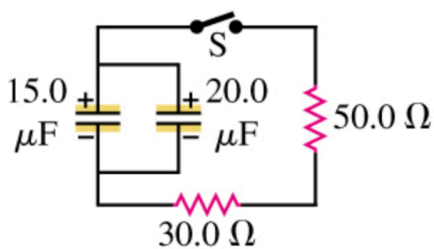

[Review](#) | [Constants](#)

Part A

How long after closing the switch S will the potential across each capacitor be reduced to 15.0 V?

Express your answer in milliseconds.

$\sqrt[n]{\square}$

$\Delta \Sigma \Phi$

↶

↷

↺

⌨

?

$t =$

ms

Submit

[Request Answer](#)

Part B

What will be the current at that time?

Express your answer in amperes.

$\sqrt[n]{\square}$

$\Delta \Sigma \Phi$

↶

↷

↺

⌨

?

$I =$

A


Problem 26.60

8 of 10

[Review I Constants](#)

Figure

1 of 1

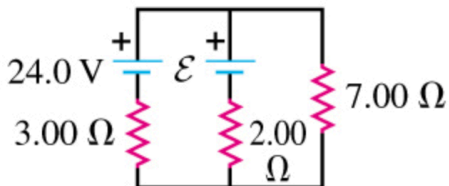

Part A

What must the emf \mathcal{E} in the figure (Figure 1) be in order for the current through the $7.00\ \Omega$ resistor to be $1.75\ \text{A}$? Each emf source has negligible internal resistance.

Express your answer with the appropriate units.

$\mathcal{E} =$

Value

Units

Submit

[Request Answer](#)


[Provide Feedback](#)

Next >

Problem 26.64

In the circuit shown in (Figure 1), $\mathcal{E} = 27.0 \text{ V}$, $R_1 = 6.00 \, \Omega$, $R_3 = 12.0 \, \Omega$, and R_2 can vary between $3.00 \, \Omega$ and $29.0 \, \Omega$.

Figure

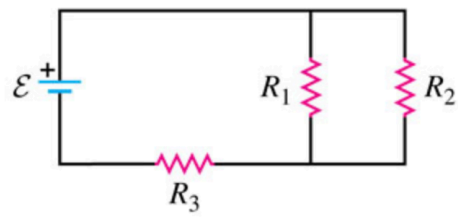

Review | Constants

Part A

For what value of R_2 is the power dissipated by heating element R_1 the greatest?

Express your answer with the appropriate units.

μA

$R_2 =$

Value

Units

Submit Request Answer

Part B

Calculate the magnitude of the greatest power.

Express your answer with the appropriate units.

μA

$P =$


Value

Units

Problem 26.66 - Enhanced - with Feedback

In the circuit shown in (Figure 1) all the resistors are rated at a maximum power of 1.40 W.

Figure 1 of 1

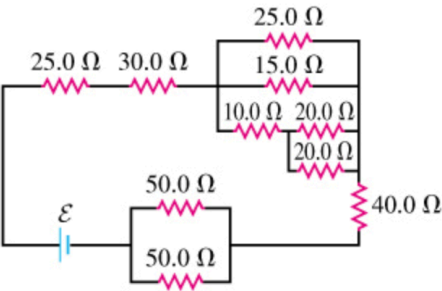

Review | Constants

Part A

What is the maximum emf \mathcal{E} that the battery can have without burning up any of the resistors?

Express your answer in volts.

$\mathcal{E} =$ V

Submit

[Request Answer](#)

[Return to Assignment](#)

[Provide Feedback](#)